

CSE 331 Computer Organizations

Project 1 – Structural Verilog & FPGA Programming

Due date: October 21, Friday 17:00

1. Design a digital circuit that detects which of the two 5-bit input numbers (**InA** and **InB**) is larger. The circuit will output a two bit signal called **Out** such that:

Situation	Out
InA = InB = 0	00
InA > InB	01
InA < InB	10
InA = InB ≠ 0	11

Use structural Verilog and Quartus.

2. Write a Verilog testbench for your circuit and simulate by ModelSim to see the correctness of your design.
3. Upload your design to DE0 FPGA board and verify it on the board.
4. *Bonus (15pts):* If you design without using any addition or subtraction process

Rules:

1. All project details (even the schematic) will be announced at next PS (October 17). So attend the PS for your own good!
2. Behavioral Verilog is not permitted. Thus, first draw your schematic on a paper.
3. Designs that are not even simulating can at most get 20pts.
4. You should show your simulation and board execution during demo hour and be graded accordingly. Demo hour will be announced on Moodle.
5. No late submissions even if 1 minute.
6. The input-output names must be exactly the same as given above.
7. *Honor code:* It is not a group project. Any cheating means at least -100 for both sides. Do not share your codes and design to any one in any circumstance. Be honest and uncorrupt not to win but because it is right!